



THE SUPERIOR UNIVERSITY LAHORE

Class Task # 02

Semester: 2 (SE, AI, DS)

Faculty of Software Engineering

Marks Obtained:

Subject: Digital Logic and Design

Total Marks:10

Teacher: Kanwal Shahbaz

Question # 01:

NAND, NOR as Universal gates

- (a) Design circuits of NOT, AND, OR, XOR, XNOR gates using NAND gate. Write their Boolean expressions and also verify from truth tables.
- (b) Design circuits of NOT, AND, OR, XOR, XNOR gates using NOR gate. Write their Boolean expressions and also verify from truth tables.